

A decorative graphic consisting of thin, grey, stylized circuit lines with small circles at the ends, extending horizontally from the left and right sides of the central black box.

# PROLOGUE

NOTHING IS GOING TO MAKE SENSE WITHOUT THIS

# WHAT IS A COMPUTER? HOW DO THEY WORK?

A Computer is any machine that can be programmed to complete tasks

Computers can be mechanical not just electronic

Digital computers use logic to execute tasks

At its most basic level a computer uses binary to compute actions



# WHAT'S BINARY

- Just like counting by tens binary is a counting system
- Instead of counting 1, 2, 3, 4 binary counts as 00, 01, 10, 11
- A rolling count
- Binary can be used to communicate values for example in electronic logic 1's are power and 0 are ground
- One binary number is called a bit a group of 8 is called a byte




# WHAT'S A LOGIC GATE?

- Many types with different functions however the three most basic are the not gate, the and gate, and the or gate


A	Q
0	1
1	0

A	B	Q
0	0	0
0	1	0
1	0	0
1	1	1

A	B	Q
0	0	0
0	1	1
1	0	1
1	1	1

   




 



# BASIC COMPUTING CHIPS


ITS ABOUT TO GET COMPLICATED

 
 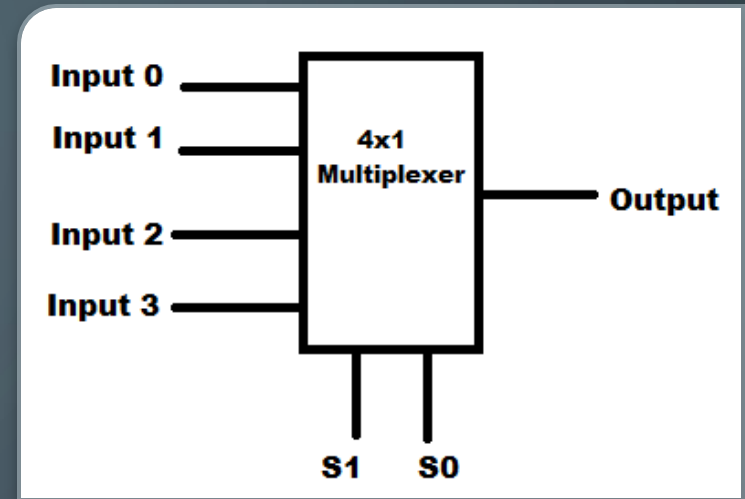
# PLEXERS

- Two types Multiplexer, and Decoders
- Multiplexers Take multiple signals and decide what signal to output (like switching the input on a tv)
- Decoders take an input signal and activate a specific output based on it






 

## MEMORY

- Many Forms the simplest is called a Latch (stores one bit)
- Registers store data near a processor
- RAM (Random Accesses Memory can quickly change values as need be)
- ROM (Read Only Memory is programed once and keeps these values often used to store instruction steps)

# LOGICAL PROCESSORS

 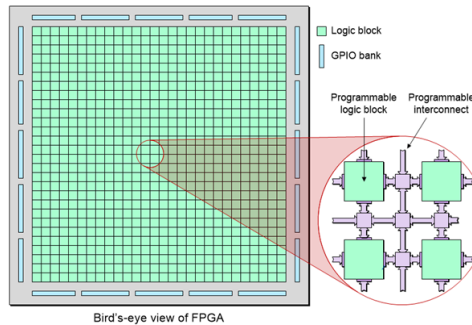 

- Gate Arrays - Reads the current data set and decides what actions are necessary
- ALU (Arithmetic Logic Unit) - Perform basic operations on given data add, subtract, multiply and divide and comparisons  $<$ ,  $>$  and bitwise operations Shifting bits left or right and finally ANDing, ORing, XORing values)
- Program Counter - Keeps track of which instructions need to be executed next






NOW THE  
REAL THING

---


BUCKLE UP

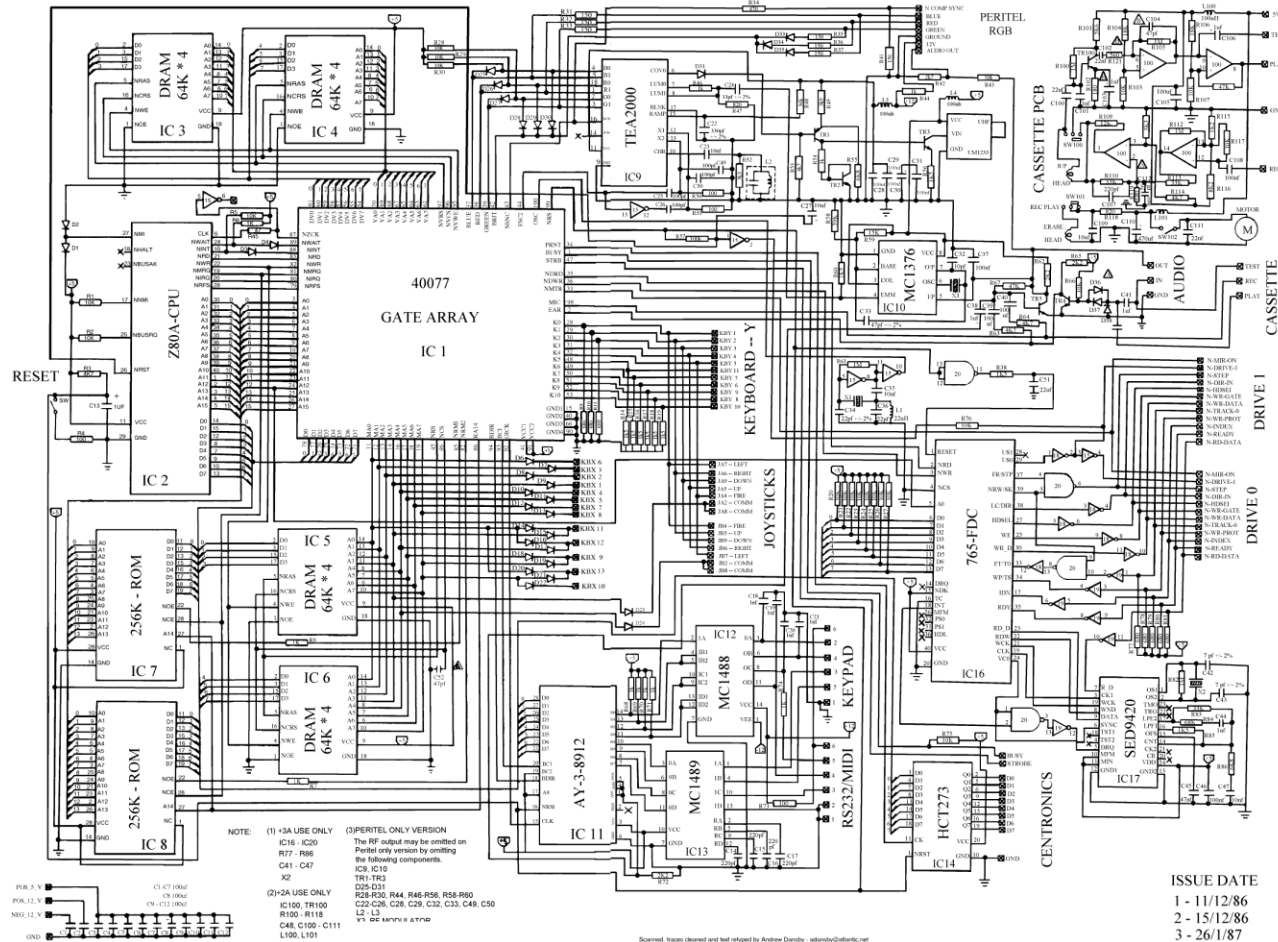



# THE SIMPLE EXPLANATION

(THANK ME LATER)

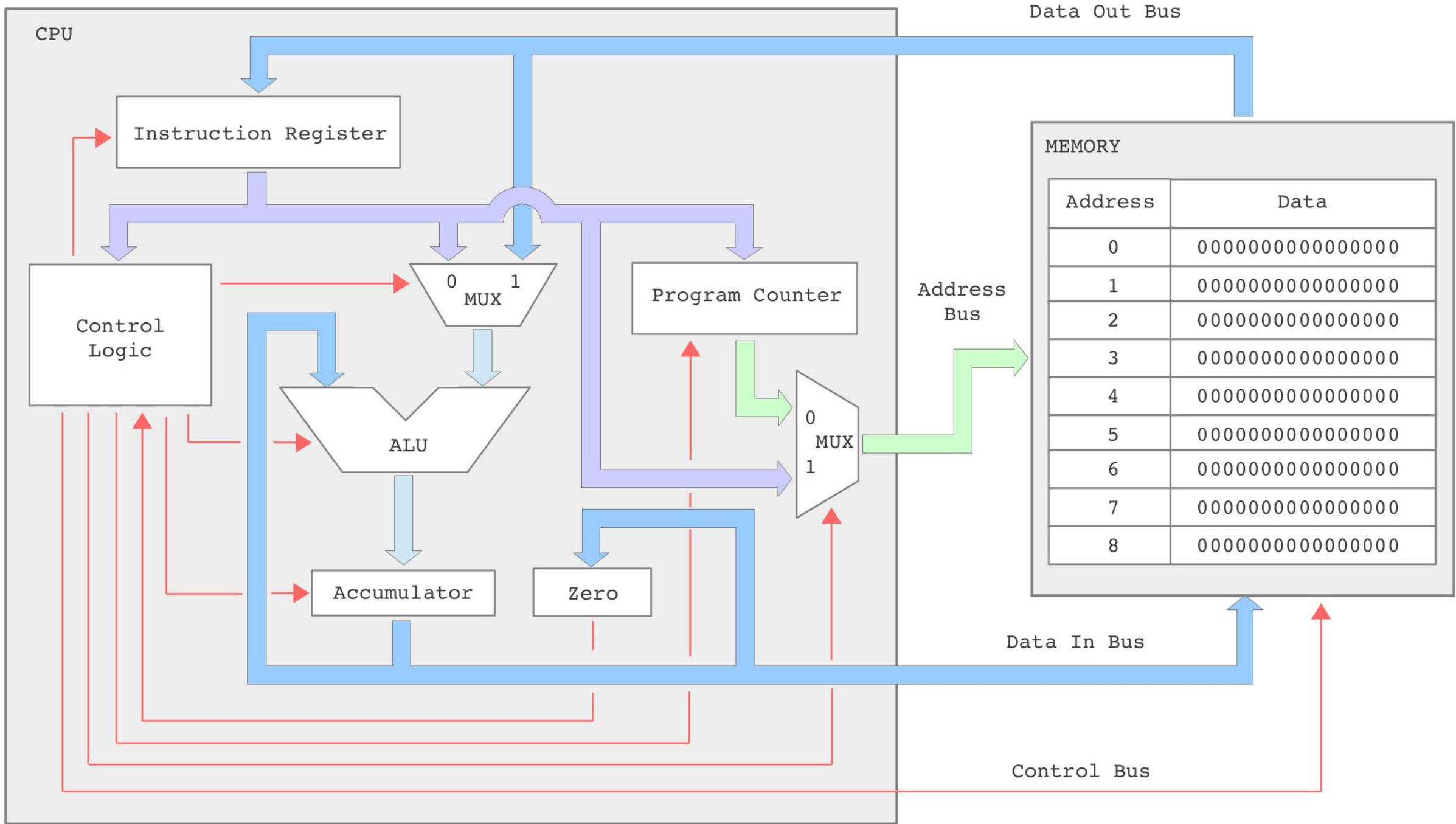



# NOW YOU KNOW THE BASICS

---

THANKS TO MWAH



A decorative graphic consisting of thin, grey, stylized circuit lines with small circles at the ends, extending horizontally from the left and right sides of the central black box.

# HOW TO BUILD A SMART PARKING GARAGE

BY: WILLIAM CONNER AND ADI LEVI

# DESIGN PROCESS

Originally the plan was to use exclusively 7400 logic (one floor nine spaces)

Decided we wanted to add the extra functionality that a PLD offers (two floors 9 per floor 18 total and full lot indicators)

Decided to highlight spots remaining to drivers because that is more useful information

Introduced random floor selection

# ABOUT OUR PROJECT

comprised of 6 IC's


Two separate  
counters 0000 to  
1001 are kept on the  
PLD

The PLD also detects  
when each floor is  
full and displays an  
indicator

Floor randomization  
is created using a  
second 555 timer set  
to a different pulse

## PART LIST

# of parts	Part name
2	555 timers
2	button
1	Gd122v10c PLD
2	7448 decoders
6	seven segment display
1	7404 inverter
12	470 $\Omega$ resistor
2	47k $\Omega$ resistor
2	22k $\Omega$ resistor

 


# HOW OUR PROJECT LOOKS LIKE AND HOW IT WORKS

Two clock signals are given to the PLD one used to drive "randomness."

The PLD keeps an individual count of each floor and drives a BDC output to decoders.

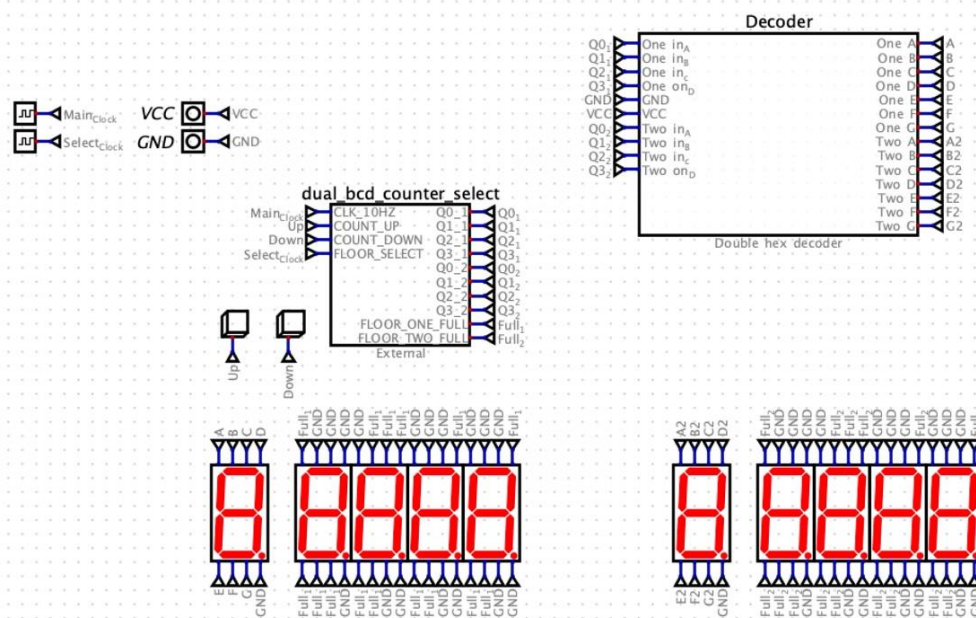
One extra pin per floor to drive the "full" signal




 
## WIRING DIAGRAM


- Designed in Digital
- Tunnels with the same names are connected (used to keep the design organized).
- Double Hex is an embedded design of two BDC to seven segment decoders.



# BLOCK DIAGRAM

# STATE TABLE AND STATE DIAGRAM

Current State	Car Enter	Car Leave	Next State Floor	Output
1001	1	X	1000	1000
1000	1	X	0111	0111
0111	1	X	0110	0110
0110	1	X	0101	0101
0101	1	X	0100	0100
0100	1	X	0011	0011
0011	1	X	0010	0010
0010	1	X	0001	0001
0001	1	X	0000	0000
0000	1	X	0000	0000
0000	X	1	0001	0001
0001	X	1	0010	0010
0010	X	1	0011	0011
0011	X	1	0100	0100
0100	X	1	0101	0101
0101	X	1	0110	0110
0110	X	1	0111	0111
0111	X	1	1000	1000
1000	X	1	1001	1001
1001	X	1	1001	1001

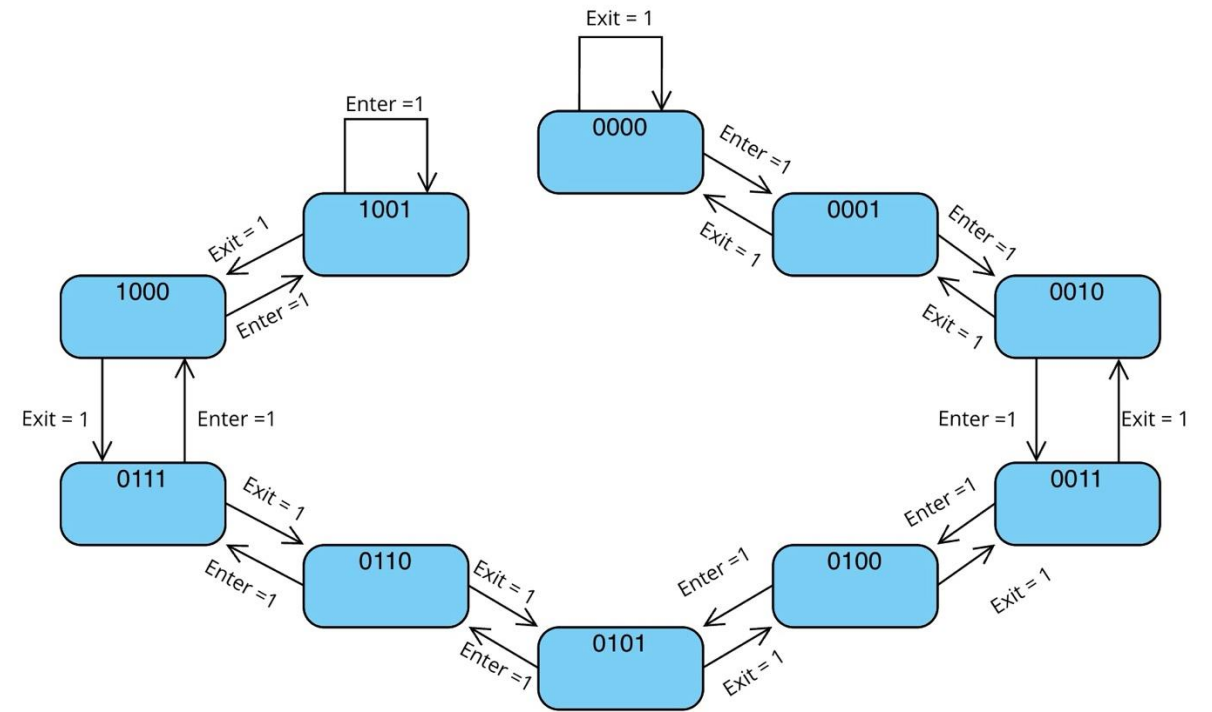

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity dual_bcd_counter_select
  Port (
    CLK_10HZ      : in  STD_LOGIC;    -- 10 Hz System Clock -> Pin 1
    CAR_LEAVE      : in  STD_LOGIC;    -- Button to count up (Car leaves) -> Pin 2
    CAR_ENTER      : in  STD_LOGIC;    -- Button to count down (Car enters) -> Pin 3
    FLOOR_SWITCH   : in  STD_LOGIC;    -- Switch to choose which floor to control -> Pin 4
    FLOOR1_BIT0    : out STD_LOGIC;    -- Bit 0 of floor one counter -> Pin 12
    FLOOR1_BIT1    : out STD_LOGIC;    -- Bit 1 of floor one counter -> Pin 13
    FLOOR1_BIT2    : out STD_LOGIC;    -- Bit 2 of floor one counter -> Pin 14
    FLOOR1_BIT3    : out STD_LOGIC;    -- Bit 3 of floor one counter -> Pin 15
    FLOOR2_BIT0    : out STD_LOGIC;    -- Bit 0 of floor two counter -> Pin 16
    FLOOR2_BIT1    : out STD_LOGIC;    -- Bit 1 of floor two counter -> Pin 17
    FLOOR2_BIT2    : out STD_LOGIC;    -- Bit 2 of floor two counter -> Pin 18
    FLOOR2_BIT3    : out STD_LOGIC;    -- Bit 3 of floor two counter -> Pin 19
    FLOOR1_FULL    : out STD_LOGIC;    -- Light when floor one full -> Pin 20
    FLOOR2_FULL    : out STD_LOGIC;    -- Light when floor two full -> Pin 21
  );
end dual_bcd_counter_select;

architecture Simplified of dual_bcd_counter_select
  signal counter1      : STD_LOGIC_VECTOR(3 downto 0) := "1001"; -- Counter for floor
one signal counter2      : STD_LOGIC_VECTOR(3 downto 0) := "1001"; -- Counter for floor
two signal car_leave_prev : STD_LOGIC := '0'; -- Previous state of CAR_LEAVE
  signal car_enter_prev  : STD_LOGIC := '0'; -- Previous state of CAR_ENTER
begin

```

# VHDL CODE EXPLAINED (BORING)

- Inputs and outputs assigned
- On start counters are initialized at 1001 (not functional)
- Detects if car leave or enter is high
- Increment when a car leaves
- Decrement when a car enters
- Floor detect 0 for floor 1 and 1 for floor 2

```

-- Counting logic
process(CLK_10HZ)
    variable car_leave_edge : STD_LOGIC := '0'; -- Detect rising edge of
CAR_LEAVEvariable car_enter_edge : STD_LOGIC := '0'; -- Detect rising edge of
CAR_ENTERbegin
    if rising_edge(CLK_10HZ) then
        -- Detect button press
        car_leave_edge := CAR_LEAVE and not car_leave_prev;
        car_enter_edge := CAR_ENTER and not car_enter_prev;
        car_leave_prev <= CAR_LEAVE;
        car_enter_prev <= CAR_ENTER;

        -- Check for button presses and update counters
        if car_leave_edge = '1' and car_enter_edge = '0' then
            if FLOOR_SWITCH = '0' then
                -- Count up floor one
                case counter1
                    when "0000" => counter1 <= "0001";
                    when "0001" => counter1 <= "0010";
                    when "0010" => counter1 <= "0011";
                    when "0011" => counter1 <= "0100";
                    when "0100" => counter1 <= "0101";
                    when "0101" => counter1 <= "0110";
                    when "0110" => counter1 <= "0111";
                    when "0111" => counter1 <= "1000";
                    when "1000" => counter1 <= "1001";
                    when others => counter1 <= "1001"; -- Max value
                end case;
            else
                -- Count up floor two
                case counter2
                    when "0000" => counter2 <= "0001";
                    when "0001" => counter2 <= "0010";
                    when "0010" => counter2 <= "0011";
                    when "0011" => counter2 <= "0100";
                    when "0100" => counter2 <= "0101";
                    when "0101" => counter2 <= "0110";
                    when "0110" => counter2 <= "0111";
                    when "0111" => counter2 <= "1000";
                    when "1000" => counter2 <= "1001";
                    when others => counter2 <= "1001"; -- Max value
                end case;
            end if;
        end if;
    end if;
end process;

```

## CONTINUED

- Detect a button press if car leave is 1 and was 0 in the last check
- Store the last state
- If a car leaves and no car enters then check the floor indicator check the current value for floor one then increase it one
- Else if floor is not 0 aka 1 then do the same but for floor 2



```

    elsif car_enter_edge = '1' and car_leave_edge = '0' then
        if FLOOR_SWITCH = '0' then
            -- Count down floor one
            case counter1
                when "1001" => counter1 <= "1000";
                when "1000" => counter1 <= "0111";
                when "0111" => counter1 <= "0110";
                when "0110" => counter1 <= "0101";
                when "0101" => counter1 <= "0100";
                when "0100" => counter1 <= "0011";
                when "0011" => counter1 <= "0010";
                when "0010" => counter1 <= "0001";
                when "0001" => counter1 <= "0000";
                when others => counter1 <= "0000"; -- Min
            end case;
        value
        else
            -- Count down floor two
            case counter2
                when "1001" => counter2 <= "1000";
                when "1000" => counter2 <= "0111";
                when "0111" => counter2 <= "0110";
                when "0110" => counter2 <= "0101";
                when "0101" => counter2 <= "0100";
                when "0100" => counter2 <= "0011";
                when "0011" => counter2 <= "0010";
                when "0010" => counter2 <= "0001";
                when "0001" => counter2 <= "0000";
                when others => counter2 <= "0000"; -- Min
            end case;
        value
        end if;
    end if;
end if;
end process;

-- Lights for when floors are full
FLOOR1_FULL <= '1' when counter1 = "0000" else '0';
FLOOR2_FULL <= '1' when counter2 = "0000" else '0';

-- Assign counter outputs
FLOOR1_BIT0 <= counter1(0);
FLOOR1_BIT1 <= counter1(1);
FLOOR1_BIT2 <= counter1(2);
FLOOR1_BIT3 <= counter1(3);
FLOOR2_BIT0 <= counter2(0);
FLOOR2_BIT1 <= counter2(1);
FLOOR2_BIT2 <= counter2(2);
FLOOR2_BIT3 <= counter2(3);


end;

```


# STILL GOING AND STILL BORING

- Similar but the opposite
- If a car enters and no car leaves than check the current state and count down one state
- When counter is 0000 than output 1 for that full signal
- Assign the counter bits to pins

# VIDEO DEMO

 


# OPPORTUNITIES FOR IMPROVEMENT

 

 1. If you hold the button it will continue to count
2. Full signal is programmed as active high on PLD
3. Starts at 0 instead of 9 when counting
4. Limited to single digits so limited only to 9 per floor





# SOLUTIONS TO DESIGN OVERSIGHTS

- 1. Using Schmitt trigger combined with a resistor and capacitor, we could smooth out the signal to clean the output or use flip-flops to store the previous states.
- 2. Change the code to have an output of 0 instead of 1 so we would not need the inverter.
- 3. Preload a 9 on the 7-segment display using a register.
- 4. We could have used 2 PLDS, one per floor to drive two 4 bit counters one for each digit